

ELECTRICAL MOTORS

6.1. THREE-PHASE POWER

The material presented so far has dealt exclusively with single-phase alternating current and voltage, that is, with single sinusoidal sources. When dealing with relatively high power it is preferable to use three-phase power. This means to use an arrangement in which three sinusoidal voltages are generated out of phase with each other. The advantages of using this arrangement are basically three:

- 1) The weight of the conductors and other components in a three-phase system is much lower than in a single-phase system delivering the same amount of power.
- 2) The three-phase system can deliver constant power (not pulsant).
- 3) Three-phase motors have nonzero starting torque.

To begin the discussion of the three-phase power, consider a three-phase source connected in wye (or Y) configuration, as shown in Figure 6.1.

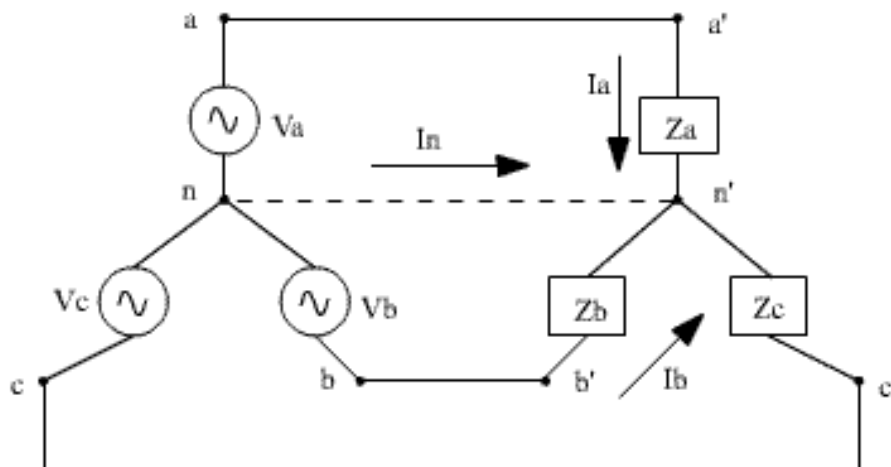


Figure 6.1. Balanced three-phase AC circuit.

Each of the three voltages is 120° out of phase with the others, so that, referring to the neutral (central) point we may write:

$$v_a = V_{a \max} \sin \omega t$$

$$v_b = V_{b \max} \sin (\omega t + 120^\circ)$$

$$v_c = V_{c \max} \sin (\omega t - 120^\circ)$$

A graph of these voltages vs time is shown in Figure 6.2.

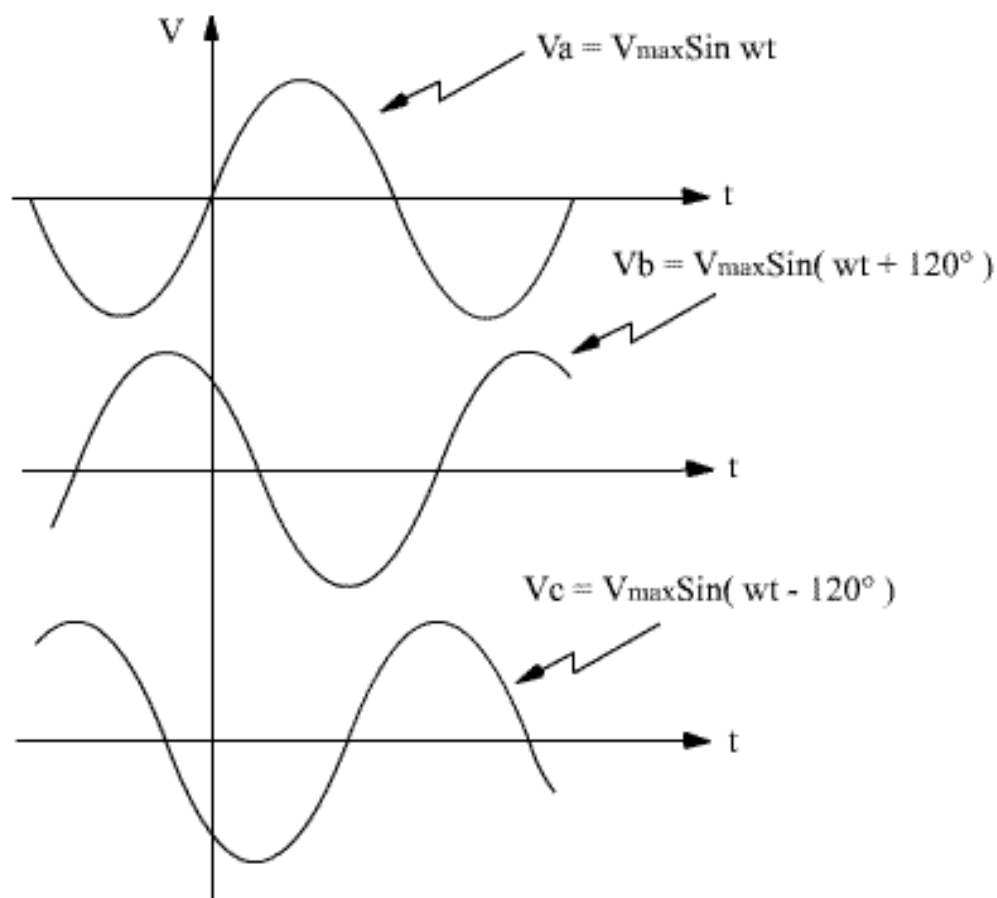


Figure 6.2. Three-phase voltages as a function of time.

A phasor representation of these voltages in a positive or abc sequence can be represented as shown in Figure 6.3, where the two axis are identified as **Re** (Real Axis), and **Im** (Imaginary Axis). A fully understanding of this representation is only possible after studying complex numbers, and is beyond the scope of this material. For the purposes of having an idea on how the phasor diagram work, it is possible to imagine that the three voltages are represented as three rotating vectors, that rotate counter clockwise with an angular velocity ω rad/sec.

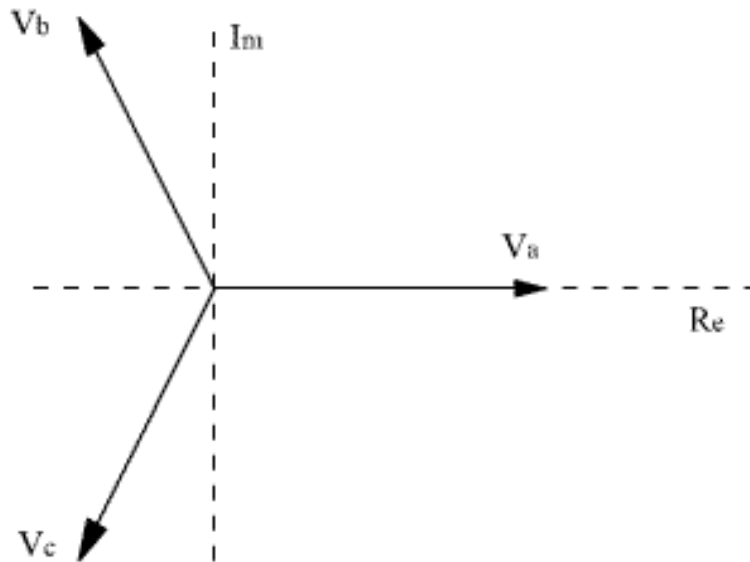


Figure 6.3. Positive sequence for balanced three-phase voltages.

In the circuit of Figure 6.1, the resistive loads are also wye-connected and balanced (i.e., equal). The voltages V_a , V_b , and V_c taken with respect to the neutral node n , are called *phase voltages* and form balanced sets in the sense that

$$V_a + V_b + V_c = 0$$

This statement is easily verified from the phasor diagram. Assuming that the voltages are numerically equal to a value V , it is possible to write

$$V - V \cos 60^\circ - V \cos 60^\circ = 0$$

A graphical solution is also possible.

The voltage difference from one line to the other is called *line voltage* (V_L) and can be also calculated using the phasor diagram as shown on Figure 6.4 where two phase voltages V_a and V_b were selected. Subtracting the two voltages it is possible to find the voltage difference, which is the line-voltage.

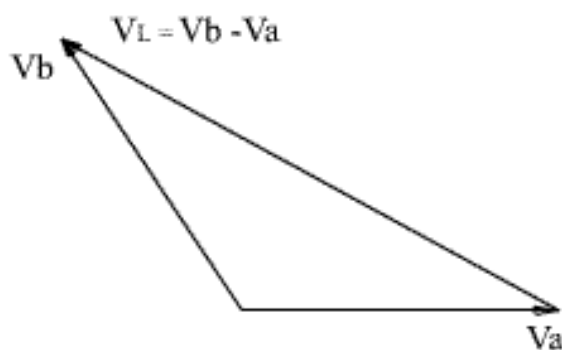


Figure 6.4. Vector addition of two phase-voltages

$$(V_L)^2 = (V_a)^2 + (V_b)^2 - 2V_a V_b \cos 120^\circ$$

$$= V^2 + V^2 + 2V^2 \cos 60^\circ$$

$$= V^2 + V^2 + 2V^2 (1/2)$$

$$= 3V^2$$

$$V_L = \sqrt{3} V$$

This means that the line-voltage is 1.73 times greater than the phase-voltage.

Example: The line-voltage in a three-phase system is 480 Volts. Find the phase-voltage.

$$V_{ph} = 480/1.73 = 277 \text{ Volts}$$

The power delivered by each voltage source to the load is calculated by

$$P_a = (v_a)(i)$$

$$= (v_a)^2/R$$

$$= (V_{\max} \sin \omega t)^2/R$$

$$= (V_{\max})^2/R \sin^2 \omega t$$

$$\sin^2 \omega t = (1 + \cos 2\omega t)/2 \text{ and } V_{\max} = \sqrt{2} V_{\text{eff}}$$

$$P_a = (V_{\text{eff}})^2/R[1 + \cos 2\omega t]$$

In this case V_{eff} is the phase-voltage effective value represented as V_{ph} .

$$P_a = (V_{\text{ph}})^2/R[1 + \cos 2\omega t]$$

For the other two phase-voltages the situation is similar, and the power delivered by each will be respectively:

$$P_b = (V_{\text{ph}})^2/R[1 + \cos(2\omega t + 120^\circ)]$$

$$P_c = (V_{\text{ph}})^2/R[1 + \cos(2\omega t - 120^\circ)]$$

The total power delivered is

$$P = P_a + P_b + P_c$$

$$= 3(V_{ph})^2/R + 3(V_{ph})^2/R[\cos 2t + \cos(2t + 120^\circ) + \cos(2t - 120^\circ)]$$

But it is easy to demonstrate that

$$[\cos 2t + \cos(2t + 120^\circ) + \cos(2t - 120^\circ)] = 0$$

From where the three-phase power is obtained as

$$P = 3(V_{ph})^2/R = \text{const.}$$

It is also possible to connect the three AC sources in a three-phase system in a so-called *delta connection*, although in practice this configuration is rarely used. What is frequently found is the balanced loads connected in a delta configuration, as shown in Figure 6.5. It should be noted that now the corresponding line-voltage appears across each impedance.

A characteristic of the loads connected in delta is that they draw 3 times as much current (and therefore absorb 3 times as much power) as a wye load with the same branch impedance.

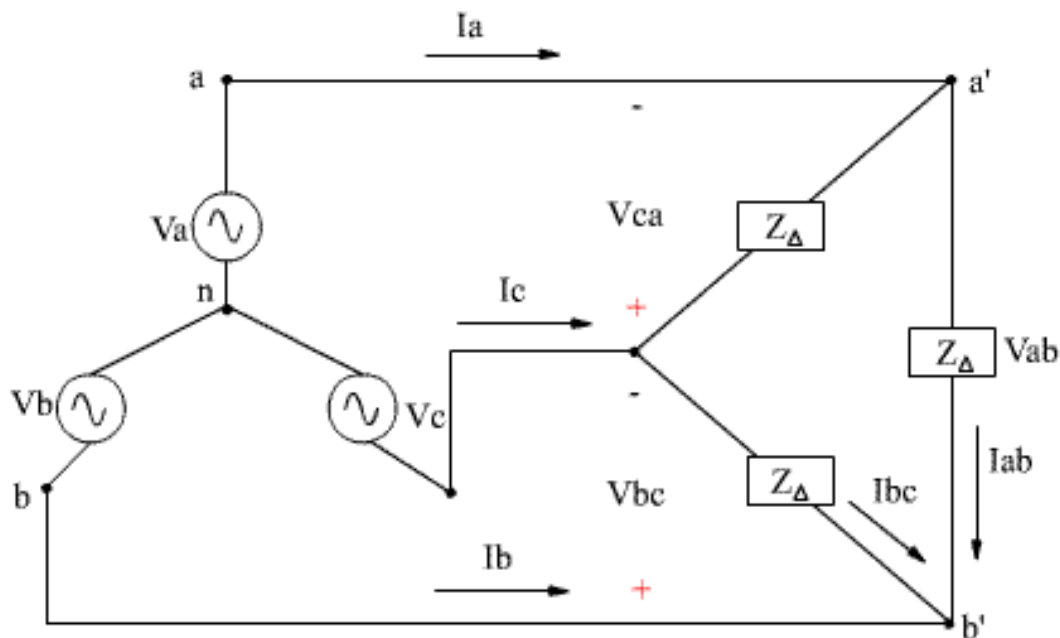


Figure 6.5. Balanced wye generators with balanced delta loads

6.2. –MOTOR WIRE CIRCUIT SELECTION

The motors are devices that convert the electrical energy into mechanical energy. There exist a big range of motors and applications. Articles 430 and 440 of the *NEC*® define the conditions of installation of motors. In the market can be found the following types of motors:

- Direct current motors
- Single-phase alternating current squirrel cage motors
- Polyphase alternating current motors
- Wound-rotor three-phase motors
- Synchronous motors
- Step motors

The basic information about the motor characteristics is obtained from the nameplate. Figure 6.6 shows a motor nameplate.

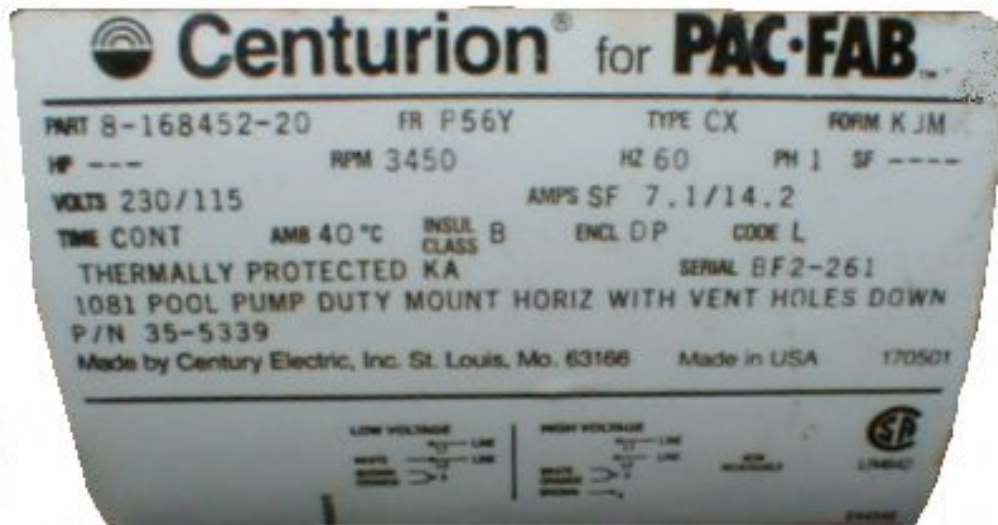


Figure 6. 6. Motor nameplate

The following information is obtained from the nameplate:

- *Frame and type.* The NEMA designation for frame designation and type
- *Horsepower.* The power rating of the motor
- *Motor code.* Designated by a letter indicating the starting current required
- *Frequency.* The number of hertz at which the motor is designed to be operated
- *Phase.* The number of phases on which the motor operates
- *RPM.* The number of revolutions per minute of the motor at full load
- *Voltage.* The voltage or voltages of operation
- *Thermal protection.* An indication of the thermal protection provided for the motor if it has any
- *Amps.* The rated current in amperes at full load
- *Duty.* The time rating of the motor showing the duty rating as continuous or as specific period of time the motor can be operated
- *Ambient temperature, or temperature rise.* The maximum ambient temperature at which the motor should be operated, or the permissible temperature rise of the motor above the ambient air at rated load
- *Service factor.* The amount of overload that the motor can tolerate on a continuous basis at rated voltage and frequency
- *Insulation class.* A designation of the insulation system used

- *NEMA design*. A letter designation for integral horsepower motors specifying the motor characteristics

Motor Circuit Conductors

There are three common motor circuits:

- Single motor
- Multiple motor
- Motor and other loads
- Hermetic compressor motor circuit (Covered in the Article 440 of the *NEC*® (Air Conditioning and Refrigerating Equipment))

The conductors that supply a single motor used in a continuous duty application shall not be less than 125% of the full-load ampere rating of the motor (Section 430-22 *NEC*®). The full-load current for each motor is obtained from the corresponding table in Article 430 of the *NEC*®. Figures 6.7 and 6.8 are partial reproductions of Tables 430-148 and 430-152 of the *NEC*®.

Horsepower	115 Volts	200 Volts	208 Volts	230 Volts
1/6	4.4	2.5	2.4	2.2
1/4	5.8	3.3	3.2	2.9
1/3	7.2	4.1	4.0	3.6
1/2	9.8	5.6	5.4	4.9
3/4	13.8	7.9	7.6	6.9
1	16	9.2	8.8	8.0
1 1/2	20	11.5	11.0	10
2	24	13.8	13.2	12
3	34	19.6	18.7	17
5	56	32.2	30.8	28
7 1/2	80	46.0	44.0	40
10	100	57.5	55.0	50

Figure 6.7. Full-Load current in Amperes, Single-Phase Alternating current motors

(From Table 430-148, *NEC*®)

Reprinted with permission from NFPA 70-1999, the National Electrical Code®, Copyright© 1998, National Fire Protection Association, Quincy, MA 02269. This reprinted material is not the referenced subject which is represented only by the standard in its entirety.

Horsepower	115 Volts	200 Volts	208 Volts	230 Volts	460 Volts
½	4.4	2.5	2.4	2.2	1.1
¾	6.4	3.7	3.5	3.2	1.6
1	8.4	4.8	4.6	4.2	2.1
1 ½	12.0	6.9	6.6	6.0	3.0
2	13.6	7.8	7.5	6.8	3.4
3	--	11.0	10.6	9.6	4.8
5	--	17.5	16.7	15.2	7.6
7 ½	--	25.3	24.2	22	11
10	--	32.2	30.8	28	14
15	--	48.3	46.2	42	21
20	--	62.1	59.4	54	27
25	--	78.2	74.8	68	34
30	--	92	88	80	40
40	--	120	114	104	52
50	--	150	143	130	65

Figure 6.8. Full-Load Current Three-Phase Alternating-Current Motors. Induction Type Squirrel Cage and Wound Rotor (Amperes). From Table 430-150, NEC®.

Reprinted with permission from NFPA 70-1999, the National Electrical Code®, Copyright© 1998, National Fire Protection Association, Quincy, MA 02269. This reprinted material is not the referenced subject which is represented only by the standard in its entirety.

Where two or more motors are used together or where one or more motors are used in combination with other loads, such as resistance heaters, etc the conductors supplying this load shall have an ampacity at least equal to the sum of the full-load current ratings of all the motors, plus 25% of the highest rated motor in the group, plus the ampere rating of other loads.

Example 6.1. Find the wires needed for feeding a 3 hp, 240 Volts, single-phase motor.

- From Figure 6.7: $I = 17$ Amps.
- The calculated value will be: $1.25 \times 17 = 21.25$ Amps.
- From Figure 3. 15: the necessary wire is a # 10 copper wire

Example 6.2. Find the feeder size for feeding three 460 Volts, three-phase motors with 10, 15, and 20 horsepower respectively.

Horsepower	Full-load current
10	14
15	21
20	27

Total current = 62

Calculated current = $62 + 0.25(27) = 68.75$ Amps

From Figure 3. 15: the necessary wire is a # 4 THWN Copper wire

Voltage Drop

If the motor is located far from the panel, the voltage drop in the conductor feeding the motor may reach some value that affect the motor work. Frequently the allowed voltage drop in the branch circuit cannot be higher than 3% to 5% of the motor name plate voltage. Because of this, the branch circuit wire size selected according to the studied rules might be not enough, and it is necessary to move to a bigger size. This will be clear with the following example.

Example 6.3. Calculate the branch motor circuit size for the motor shown in Figure 6.9. The motor nameplate characteristics are as follows: single phase, 230 V, 10 HP. The maximum allowable voltage drop in the conductors is 5% of the nameplate voltage.

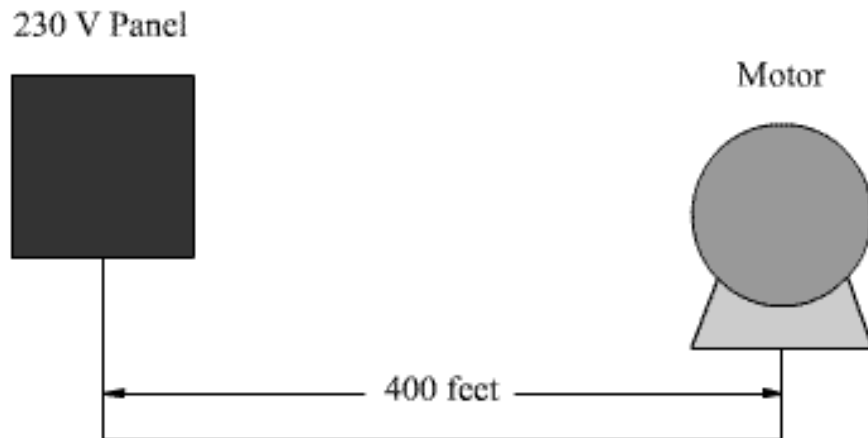


Figure 6.9. Motor Circuit.

According to Table 430-148, *NEC*® (fig. 6.7), this motor consumes 50 Amp. The necessary wire ampacity is $50 \times 1.25 = 62.5$ Amp. The selected copper wires are two # 6 THHN. From Table 8, *NEC*® the resistance of this wire is 0.51 ohm/1000 ft.

The total resistance in the conductors will be: $R = 0.51 \times 800/1000 = 0.408$.

The voltage drop is: $V = 0.408 \times 50 = 20.4$ Volts.

The maximum permitted voltage drop is: $230 \times 0.05 = 11.5$ Volts.

The selected wire size cannot be used because the actual voltage drop is higher than the permitted. Then it is necessary to use a bigger wire.

If two # 4 Cu. Wires are used, The total resistance is $0.32 \times 800/1000 = 0.25$, and the voltage drop $0.25 \times 50 = 12.5$ Volts.

Using two # 3 THHN Cu. Wires:

$$R = 0.24 \times 800/1000 = 0.19$$

$$V = 0.19 \times 50 = 9.5 \text{ Volts.}$$

Due to the distance, it is necessary to use two # 3 Cu. Wires for this motor.

6.3. OVERCURRENT PROTECTION

In a single motor circuit, the essential parts are: the branch-circuit conductors, the disconnecting means, the branch-circuit short-circuit and ground-fault protective devices, and the motor overload protective devices.

The branch-circuit short-circuit and ground-fault protective device may be a fuse or a circuit breaker and is required to be capable of carrying the starting current of the motor without opening the circuit. The motor branch-circuit, short-circuit and ground-fault protection is treated in part D of Article 430, *NEC*®. There are specified devices intended to protect the motor branch –circuit conductors, the motor control apparatus, and the motors against over-current due to short-circuits or grounds for motors under 600 Volts.

The maximum values for the protective devices are shown in Figure 6.10 which is a partial reproduction of Table 430-152, *NEC*®.

Percentage of Full-Load Current

Type of Motor	Nontime Delay Fuse	Dual Element (Time-Delay) Fuse	Instantaneous Trip Breaker	Inverse Time Breaker
Single-phase motors	300	175	800	250
AC polyphase motors other than wound-rotor				
Squirrel cage Other than Design E	300	175	800	250
Design E	300	175	1100	250

Figure 6.10.. Maximum Rating or Setting of Motor Branch-Circuit Short-Circuit and Ground-Fault Protective Devices.

Reprinted with permission from NFPA 70-1999, the National Electrical Code®, Copyright© 1998, National Fire Protection Association, Quincy, MA 02269. This reprinted material is not the referenced subject which is represented only by the standard in its entirety.

Figure 6.11 shows the essential elements in a single motor circuit.

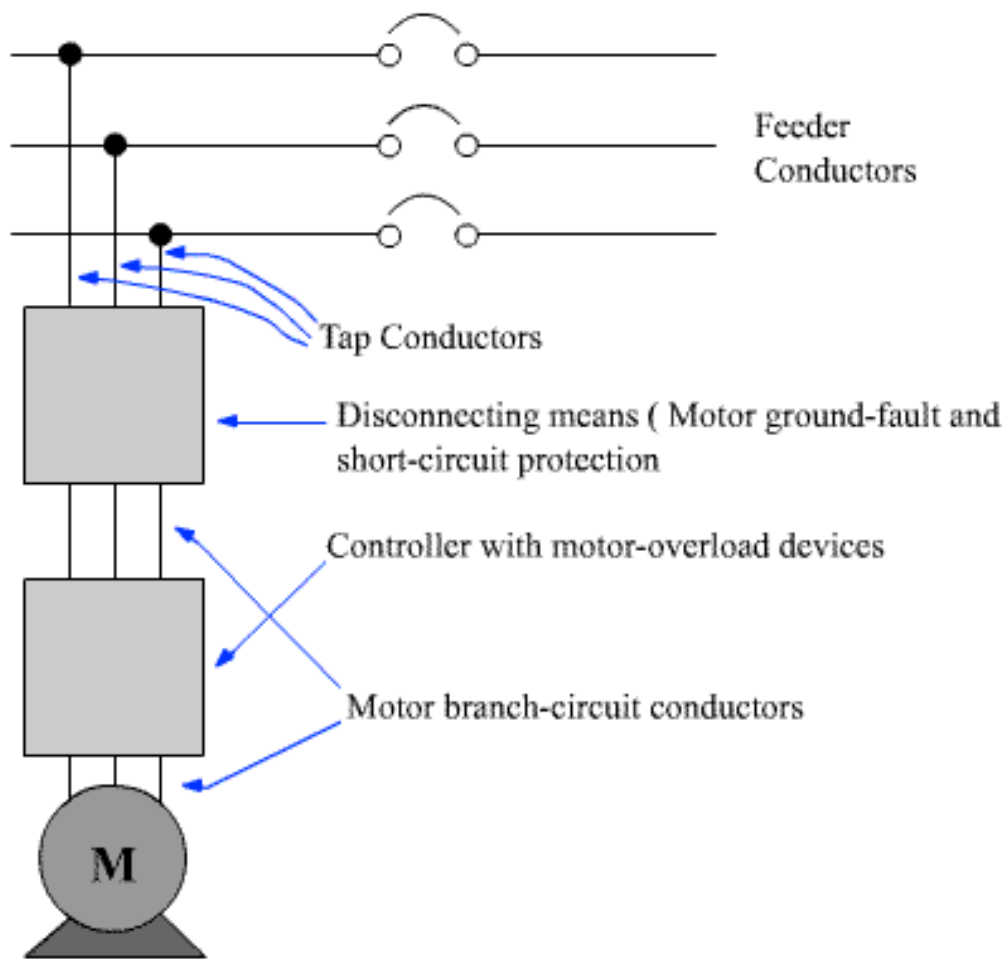


Figure 6.11 A motor branch circuit showing the essential parts: branch-circuit conductors, disconnecting means, branch-circuit over-current protection, and motor overload devices.

6.4. REVIEW QUESTIONS

- 6.1. What are the advantages of the three-phase power?
- 6.2. In a WYE connection, if the phase voltage is 120 Volt. Calculate the line voltage.
- 6.3. Calculate the power dissipated by a three-phase load for $V_{ph} = 120$ Volt and $R_L = 50$ ohms.
- 6.4. Enumerate three types of motors.
- 6.5. The greatest allowable voltage drop for a 1 hp, 120 V, 3 hp motor is 10% of the name plate. The motor is located 250 ft. apart from the panel. Find the needed wire.
- 6.6. The *NEC*® requires that motors shall be supplied by branch circuit conductors having _____% of full-load current.
- 6.7. Find the circuit conductors supplying a 20 hp, 230 V, 3 hp squirrel-cage motor.


6.8. Three resistive balanced loads are connected to a 480 Volt (line voltage), 3-phase circuit. What is the total power of the circuit in kW for a 40 Amp current?

6.9. In a motor nameplate, the label FLA means _____.


6.10. In a motor nameplate the label SF means _____.

6.11. The following loads are connected to a feeder: one 1hp, 240 V, 5 hp motor, one 1hp; one 1hp, 240 V, 3 hp motor and 10 amp receptacles/lights. Find the feeder needed wire.

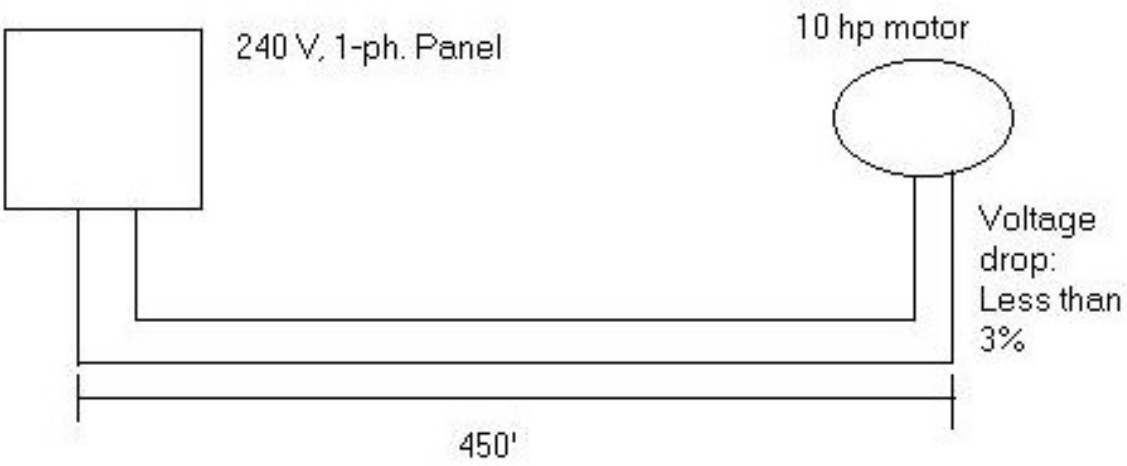6.12. Calculate the wire size for the following installation:



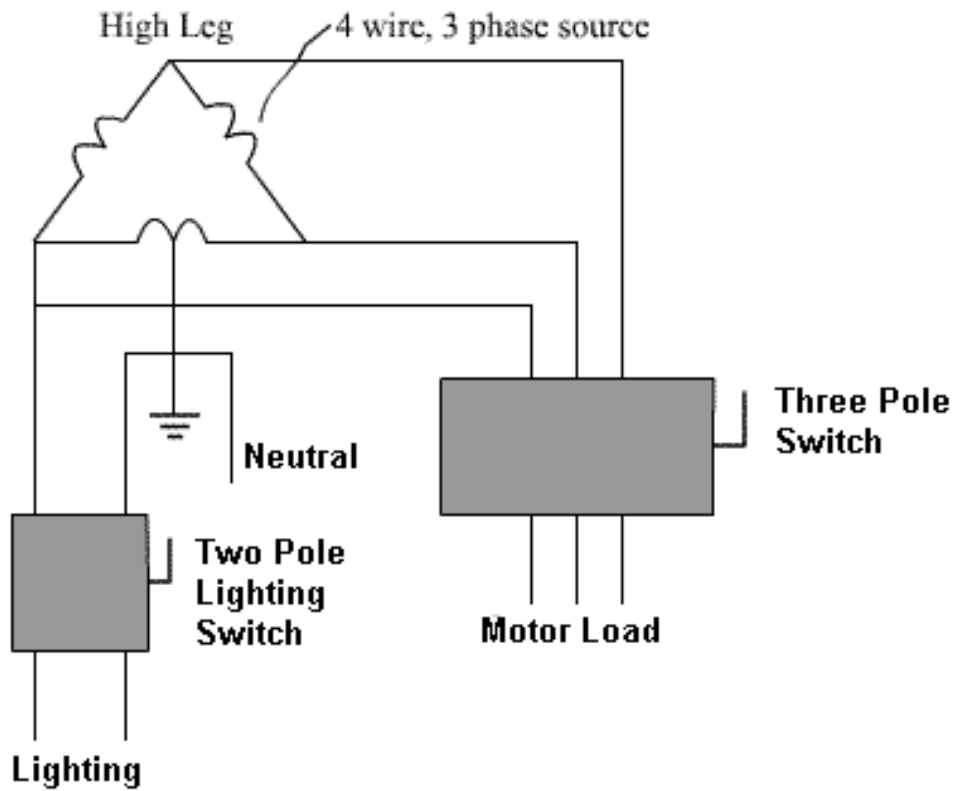6.13. A pump station has a 10 kVA lighting load, one 3 hp. motor, two 5 hp motors and one 15 hp motor. All the loads are fed from a delta 3 ph., 240 V source, as shown in the Figure below.



- Draw a circuit representing the motors and lights connected to the source, including all the switches and over-current devices needed.
- Find the load for each feeder and the protection devices rating.

National Electrical Code® and NEC® are registered trademarks of the National Fire Protection Association, Inc., Quincy, MA 02269